



CS61C: Hardware & CPU Review

CS61C Fall2007 - Discussion #11

Greg Gibeling

11/6/2007

CS61C Discussion #11

1




Combinational Logic

- Optimization & Simplification
 - Constant Propagation
 - Common Subexpressions
 - Truth Tables
 - Don't Care Inputs & Outputs (Not the same!)
- Special Gates
 - OR: Detect 0
 - AND: Detect 1
 - XOR: Compare, Conditional Invert, Add
 - Mux, NAND: Universal
- Delay & Cost
 - Critical Path (Quiz)
 - Gate Count (Proj4 in simple gates!)

11/6/2007

CS61C Discussion #11

2

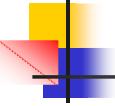


State

- Registers
 - Delay of one clock cycle
 - Storage (assuming Enable control)
 - Connection through time
- Datapath
 - Generally registers are data storage
 - Pipeline registers?
- FSMs
 - Bubble & Arc Diagrams
 - State & Output Encoding
 - Single register, two CL blocks

11/6/2007

CS61C Discussion #11

3

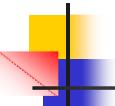


General SDS Design

- Datapath
 - Value Registers
 - Mostly Combinational Logic
 - Almost all of it \sim 32b (or some fixed #) wide
 - Mux & Control Inputs
- Control
 - Decode – Sum of Products
 - Stateful Control (Multi-cycle Designs)
- How To
 - Draw the schematic
 - Work out the timing diagrams
 - Code in Verilog
 - Test

11/6/2007

CS61C Discussion #11

4

 


Pipelining

- Basic Tradeoff
 - Throughput: increased
 - Latency: unaffected (slight increase, why?)
- Design
 - Add registers in the middle of the proc
 - Forwarding logic
- Dependencies
 - Control (Branches)
 - Data
 - RAW – True Data Dependence
 - WAW – Not a problem?
 - WAR – Not a problem?

11/6/2007

CS61C Discussion #11

5

 

Questions/Examples

- Questions
 - Proj4 Clarifications
 - Why x86?
 - Variable Latency Instructions
- Problems
 - Memory-To-Memory Processor
 - Implement MicroCode
 - Design Out of Order Processor (OOO/Tomasulo)

11/6/2007

CS61C Discussion #11

6